

Electrical and Computer Engineering  
University of Thessaly (UTH)

## **ECE327 - VLSI**

Fall Semester — Educational year 2022-2023

### **Lab01**

## **CMOS Inverter Design & Simulation**

Georgios Kapakos - AEM: 03165

# Contents

<b>1</b>	<b>Exercise 1: CMOS Inverter Schematic</b>	<b>3</b>
<b>2</b>	<b>Exercise 2: Modified SPICE File and Timing Measurements</b>	<b>4</b>

## Introduction

This assignment focuses on the design, extraction, and simulation of a CMOS inverter using SPICE. The tasks involve creating a schematic, extracting it into a SPICE netlist, verifying transistor connections, and performing transient analysis to measure key timing parameters such as propagation delays and rise/fall times. The goal is to understand the behavior of CMOS circuits and validate their functionality through simulation and graphical representation.

### 1 Exercise 1: CMOS Inverter Schematic

Initially, the .spice file is extracted as follows. After extraction, the resulting file cannot run directly in NGSPICE, so it requires modification.

 


Figure 1: CMOS Inverter

From the code below, we conclude that the transistor terminals are correctly connected:

- **nMOS (M1000)**: Drain to output, gate to input, source and bulk to vdd.
- **pMOS (M1001)**: Drain to output, gate to input, source and bulk to ground.

## exercise1.spice

```
gkapakos@LAPTOP-L3SKMRC7: /mnt/c/WINDOWS/system32
* SPICE3 file created from exercise1.ext - technology: scmos
.option scale=1u
M1000 out in vdd vdd pfet w=3 l=2
+ ad=19 pd=18 as=19 ps=18
M1001 out in gnd gnd nfet w=3 l=2
+ ad=19 pd=18 as=19 ps=18
C0 in 0 3.64fF
```

Figure 2: Spice code for the circuit

## 2 Exercise 2: Modified SPICE File and Timing Measurements

The modified .spice file is prepared for transient analysis. To measure propagation delays ( $t_{phl}$ ,  $t_{plh}$ ) and rise/fall times ( $t_{rise}$ ,  $t_{fall}$ ), we adjust the models, add .tran commands, and use .meas to capture the required timing values.

## exercise1.spice

```
gkapakos@LAPTOP-L3SKMRC7: /mnt/c/WINDOWS/system32/spice_exercices

Circuit: ****askisi 1****

Scale set
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Warning: vin: no DC value, transient time 0 value used

Initial Transient Solution
-----

Node                                Voltage
----                                -
vs                                  2.5
out                                2.5
in                                  0
vin#branch                          0
vdd#branch                         -5.27718e-12

No. of Data Rows : 620

Measurements for Transient Analysis

t_phl      = 6.288096e-10 targ= 7.538096e-10 trig= 1.250000e-10
t_plh      = 7.607324e-10 targ= 1.885732e-09 trig= 1.125000e-09
t_rise     = 5.623999e-10 targ= 2.159177e-09 trig= 1.596777e-09
t_fall     = 3.037825e-10 targ= 9.487381e-10 trig= 6.449556e-10
```

Figure 3: Measurements for the transient analysis in spice.

## Timing Measurements

### Rise Time ( $t_{rise}$ )

To calculate  $t_{rise}$ , we determine the output rise time from 10% of vdd (0.25V) to 90% of vdd (2.25V) during the first rising edge (rise = 1). Using the points:

- $x_2 = 300, x_1 = 100, y_2 = 2.25, y_1 = 0.25$

Slope:

$$\lambda_1 = \frac{y_2 - y_1}{x_2 - x_1} = \frac{2}{200} = 0.01$$

Equation:

$$y = 0.01x - 0.75$$

- For  $y = 0$ :  $x = 75$  ps (10% of vdd)
- For  $y = 2.5$ :  $x = 325$  ps (90% of vdd)

### Fall Time ( $t_{fall}$ )

To calculate  $t_{fall}$ , we determine the output fall time from 90% of vdd (2.25V) to 10% of vdd (0.25V) during the first falling edge (fall = 1). Using the points:

- $x_2 = 1150, x_1 = 950, y_2 = 0.25, y_1 = 2.25$

Slope:

$$\lambda_1 = \frac{y_2 - y_1}{x_2 - x_1} = \frac{-2}{200} = -0.01$$

Equation:

$$y = -0.01x + 11.75$$

- For  $y = 0$ :  $x = 1175$  ps (10% of vdd)
- For  $y = 2.5$ :  $x = 925$  ps (90% of vdd)

### Propagation Delays ( $t_{phl}$ and $t_{plh}$ )

- $t_{plh}$ : Time between 50% of vdd (1.25V) at the input (first fall, fall = 1) and 50% of vdd (1.25V) at the output (first rise, rise = 1).
- $t_{phl}$ : Time between 50% of vdd (1.25V) at the input (first rise, rise = 1) and 50% of vdd (1.25V) at the output (first fall, fall = 1).

## Graphical Representation of CMOS Inverter

 


Figure 4: CMOS Inverter plot

## Conclusion

This assignment successfully demonstrates the design and simulation of a CMOS inverter. The extraction process verified correct transistor connections, while the transient analysis provided accurate measurements of rise/fall times and propagation delays. The calculated values and waveforms confirm the inverter's functionality, offering insights into CMOS circuit performance and timing characteristics critical for VLSI design.